


Building Energy-Efficient Circuits with NEMS Devices

Vladimir Stojanović (MIT)

in collaboration with

Tsu-Jae King Liu, Elad Alon (UC Berkeley)



Dejan Marković (UCLA)

 

UCLA

May 23-24, 2010


Subthreshold Leakage: Game Over for CMOS

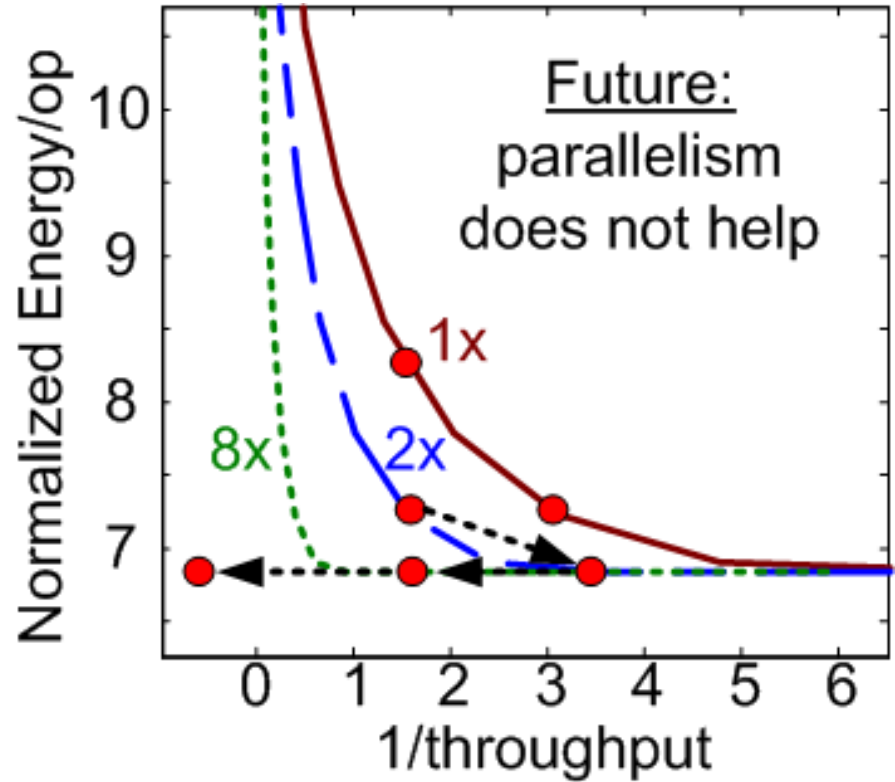 


- ❑ Leakage and sub-threshold slope define minimum energy/op for CMOS
- ❑ Parallelism cannot reduce power/throughput if already operating at minimum energy

NEM Relays to the Rescue

Measured MEM Switch I-V Curve



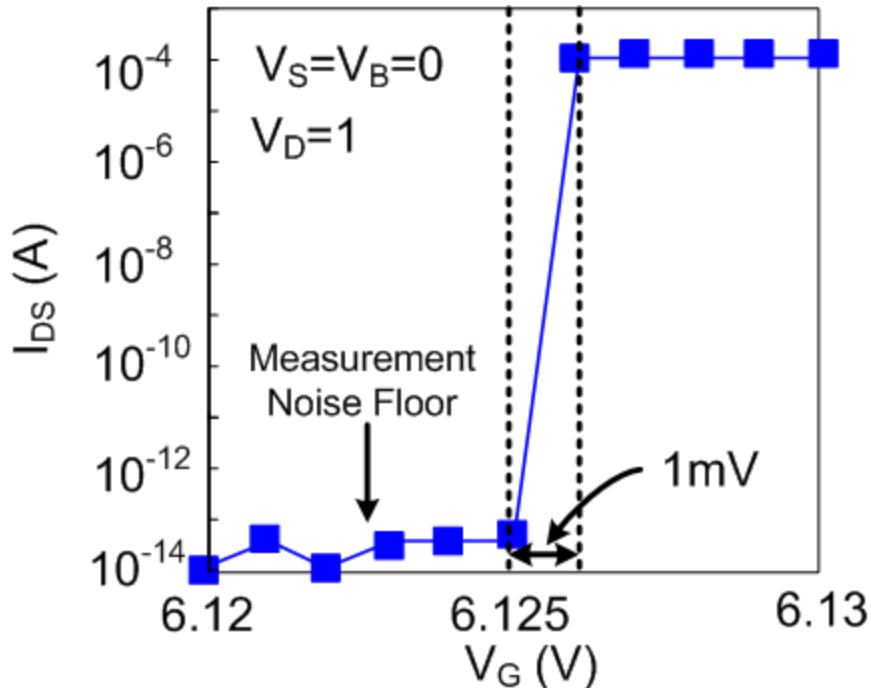


MEM Switch Energy vs. V_{DD}

 


- ❑ NEM relays show zero leakage & sharp sub-threshold slope
- ❑ Could potentially enable reduced E/op with scaling
- ❑ E_{min} set by contact bond energy
 - ~ 4 aJ/switch (10x better than 65nm CMOS)

NEM Relay Structure and Operation

   

A-A' cross-section: *off-state*

 

A-A' cross-section: *on-state*

OFF Relay:



$$|V_{gb}| < V_{po} \text{ (pull-out voltage)}$$

ON Relay:

$$|V_{gb}| > V_{pi} \text{ (pull-in voltage)}$$

NEM Relay as a Logic Element




“NMOS” “PMOS”

  

BUF




INV

   


- ❑ 4-terminal design mimics MOSFET operation
 - Electrostatic actuation is ambipolar
- ❑ Non-inverting logic is possible
 - Actuation independent of source/drain voltages

Digital Circuit Design with NEMS

CMOS: 30 transistors

 


NEMS: 12 switches

 

- ❑ CMOS: delay set by electrical time constant
 - Quadratic delay penalty for stacking devices
 - Buffer & distribute logical/electrical effort over many stages
- ❑ NEMS: delay dominated by mechanical movement
 - Can stack ~100-200 devices before $t_{d,elec} \approx t_{d,mech}$
 - So, want all to switch simultaneously
 - → Implement logic as a single complex gate


Need to Compare at Block Level

CMOS: 30 transistors

 

4 gate delays →


NEMS: 12 relays

 

1 mechanical delay →

- ❑ Delay Comparison vs. CMOS
 - Single mechanical delay vs. several electrical gate delays
 - For reasonable load, NEMS delay unaffected by fan-out/fan-in
- ❑ Area Comparison vs. CMOS
 - Larger individual devices
 - But often need fewer devices to implement same function

Example: 32-bit NEMS Adder

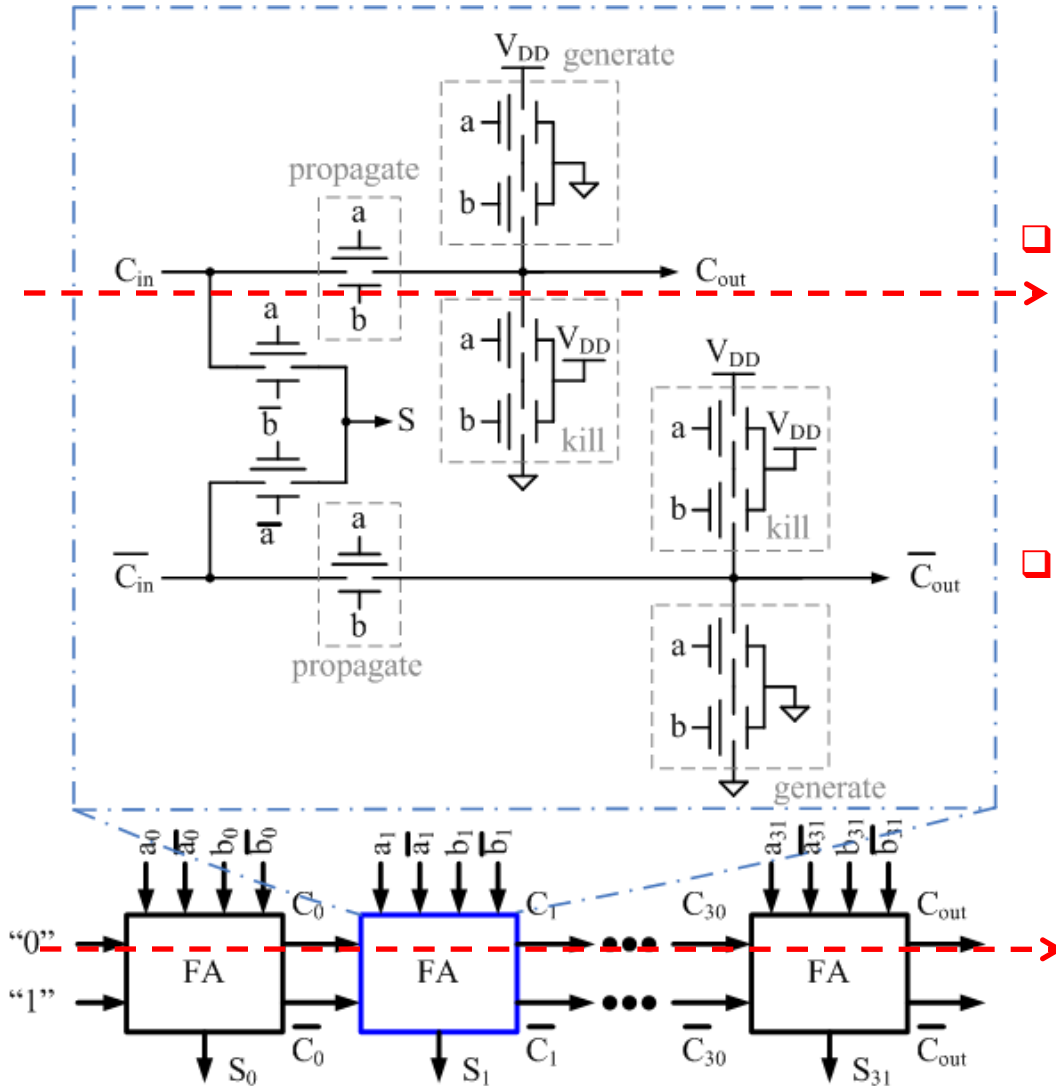


- ❑ Ripple carry configuration
 - Cascade full adder cells to create larger complex gate

- ❑ Stack 32 NEMS, but still single mechanical delay

Scaled NEMS vs. CMOS Adders

Energy/op vs. Delay/op across V_{dd}

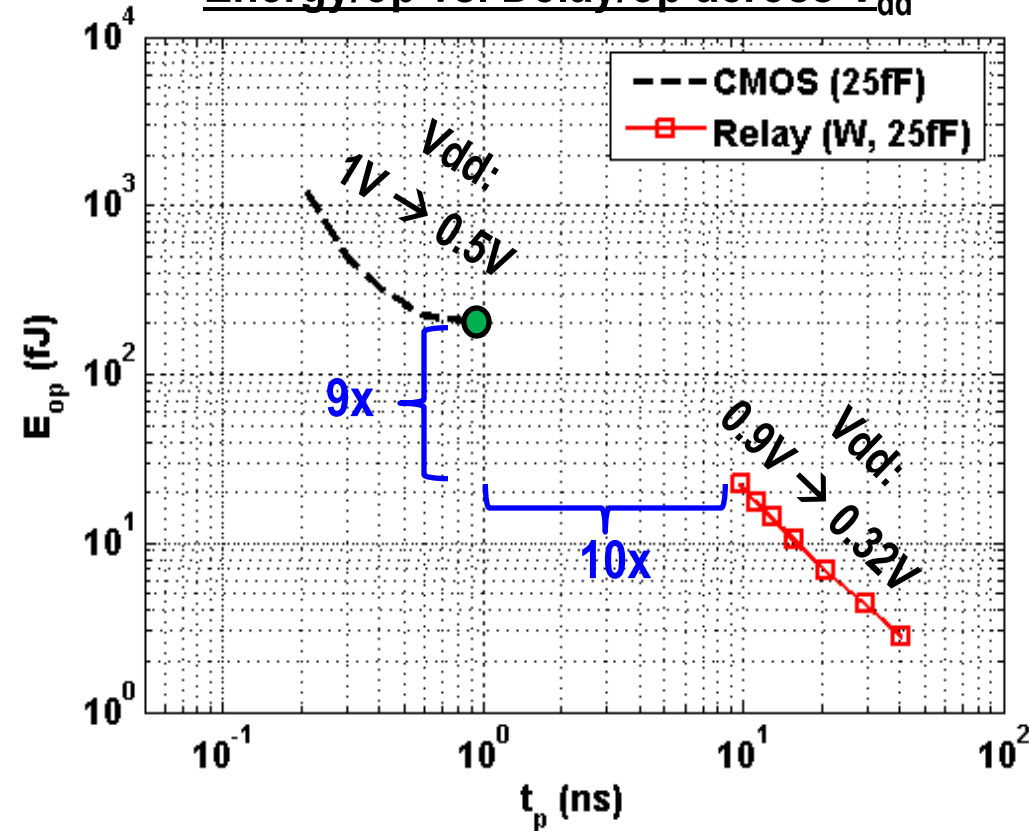

- Compare vs. Sklansky CMOS adder*

- 90nm technology

- 30x less capacitance

- Lower device C_g , C_d

- Fewer devices

- 2.4x lower V_{dd}

- No leakage energy


- For similar area: >9x lower E/op, >10x greater delay

F. Chen *et al.*, "Integrated Circuit Design with NEM Relays," *ICCAD 2008*

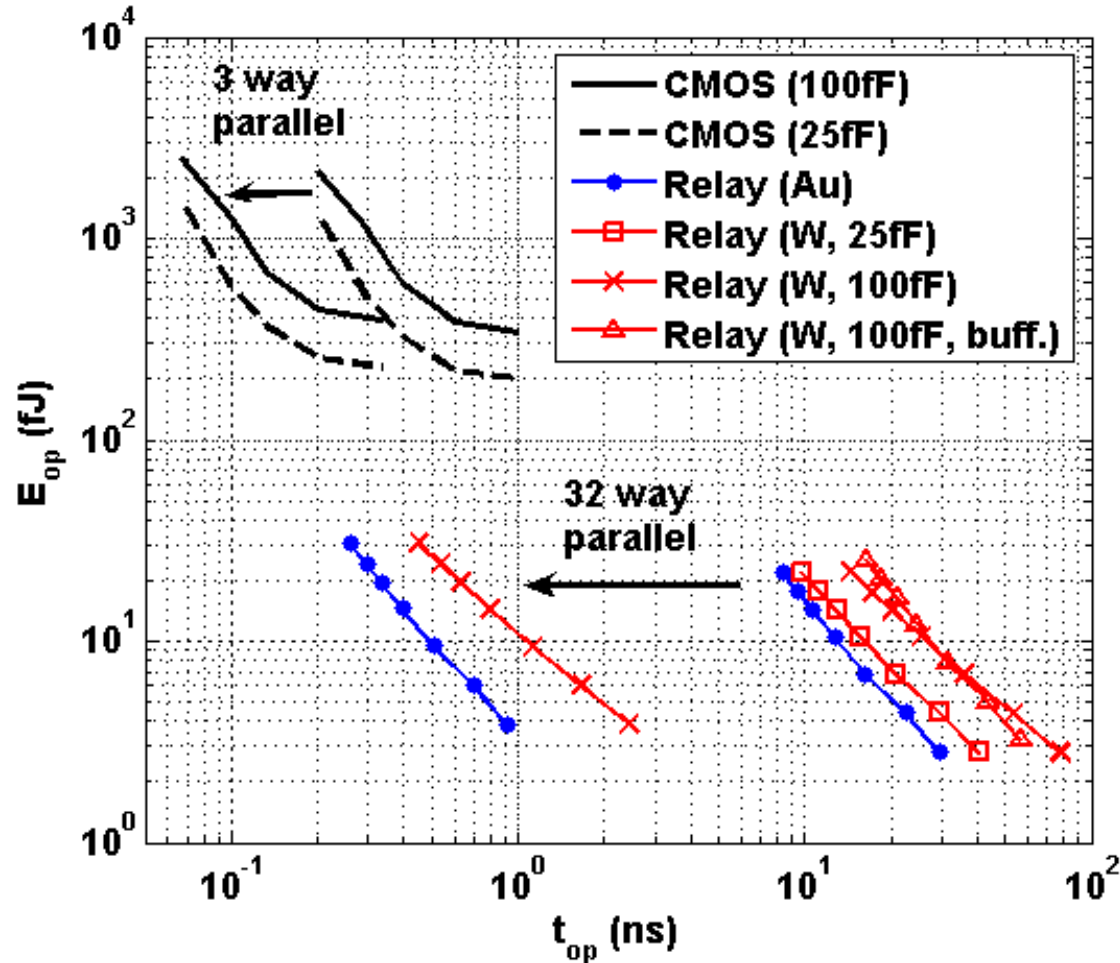*D. Patil *et al.*, "Robust Energy-Efficient Adder Topologies," in Proc. 18th IEEE Symp. on Computer Arithmetic (ARITH'07).

Parallelism: Trade Area for Performance


Energy/op vs. Delay/op across V_{dd} & C_L



- Can extend energy benefit up to GOP/s throughput
 - As long as parallelism is available
- Area overhead bounded
 - CMOS needs to be parallelized at some point too

Contact Resistance

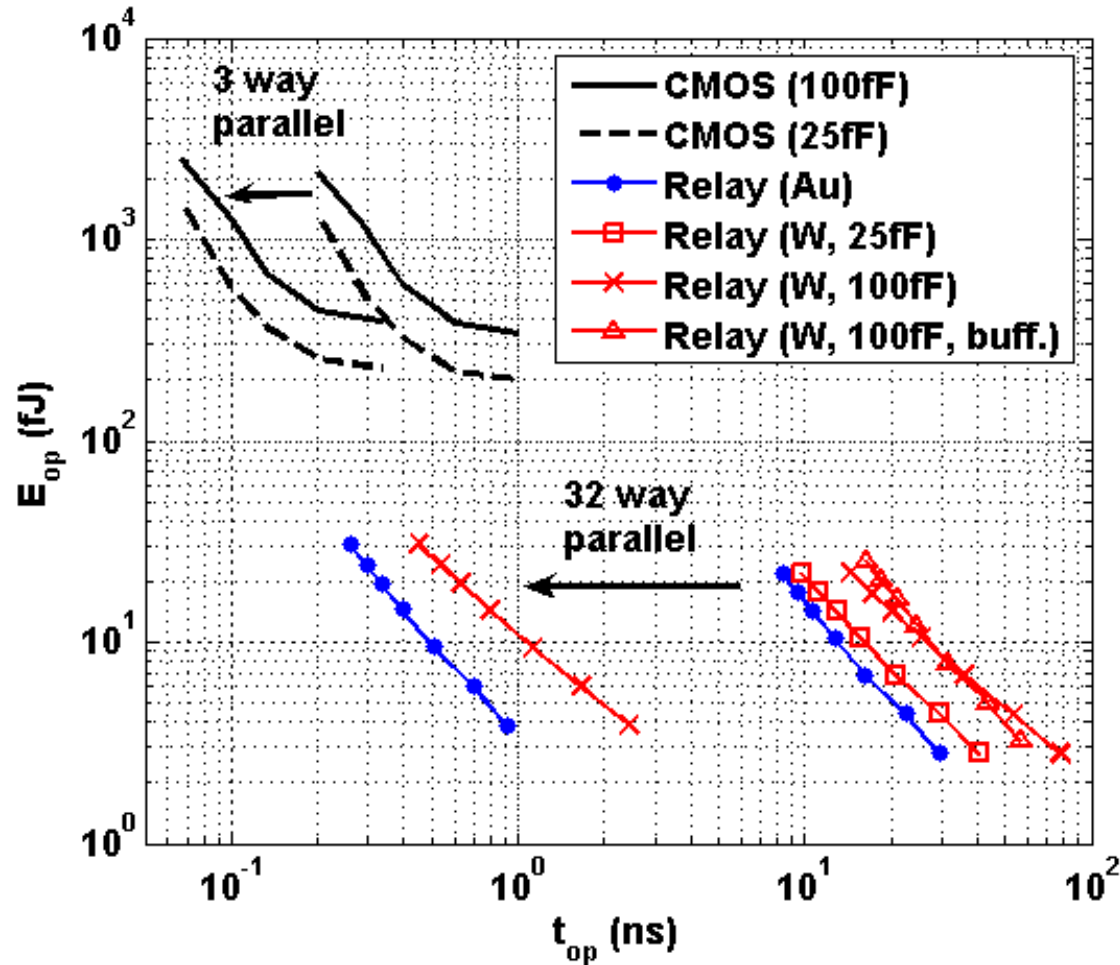Energy/op vs. Delay/op across V_{dd} & C_L










□ Low contact R not critical

□ Good news for reliability...


□ Relays with W contacts lived through 65 B cycles

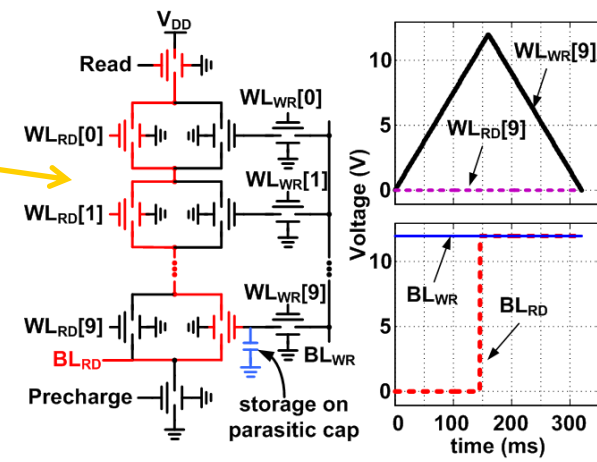    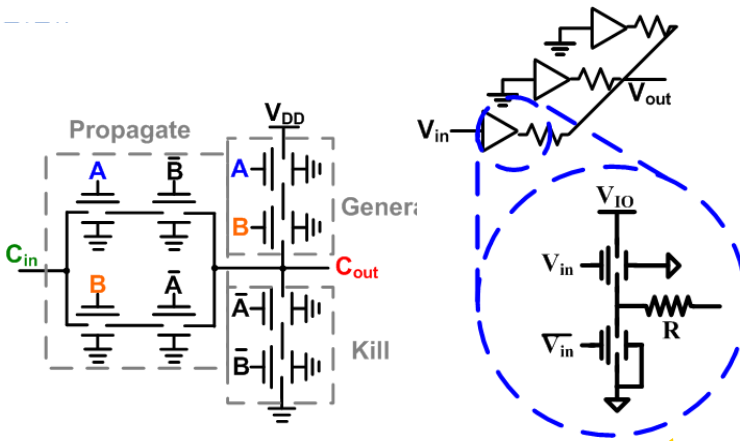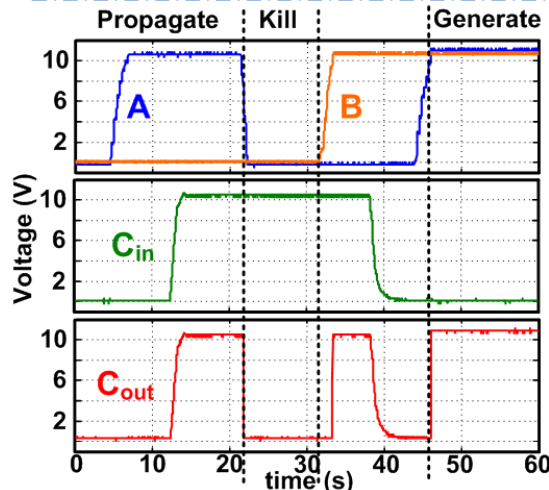NEM Relay-based Circuits: First Test-chip




F. Chen et al., "Demonstration of Integrated Micro-Electro-Mechanical Switch Circuits for VLSI Applications," *ISSCC 2010*.


NEM Relay Scaling – Next Design

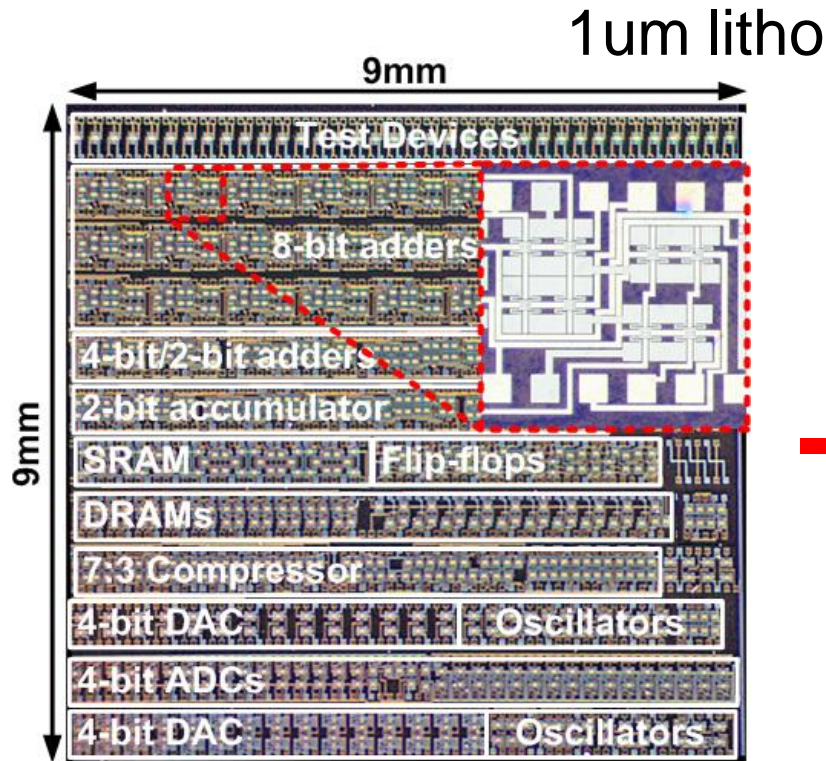


0.25um litho

 

NEM relay size
120um x 150um

 

Scaled NEM relay
20um x 20um

 

Conclusions

- ❑ NEMS unique features enable energy scaling beyond-CMOS
 - Nearly ideal $I_{\text{on}}/I_{\text{off}}$
 - Switching delay largely independent of electrical τ
 - Need to adapt circuit design style
- ❑ Reliability improving
 - Circuit level insights critical (contact R)
 - Demonstrated simple circuits
 - Can start thinking about building more complex systems
- ❑ Potentially order of magnitude lower E/op than CMOS
 - Next steps: scaling and improved device design, testing larger digital blocks

Acknowledgements

□ Circuit design

- Fred Chen, Hossein Fariborzi
- Matthew Spencer, Abhinav Gupta
- Cheng Wang, Kevin Dwan

□ Device design

- Hei Kam, Rhesa Nathanael, Vincent Pott, Jaeseok Jeon

□ Sponsors

- DARPA NEMS program
- FCRP (C2S2, MSD)
- MIT CICS
- Berkeley Wireless Research Center
- NSF