


Design Methodologies and Automation for Relay-Based Circuits

Dejan Marković (UCLA)


in collaboration with

Elad Alon, Tsu-Jae King Liu (UC Berkeley)

Vladimir Stojanović (MIT)

 


Relay VLSI Design Infrastructure

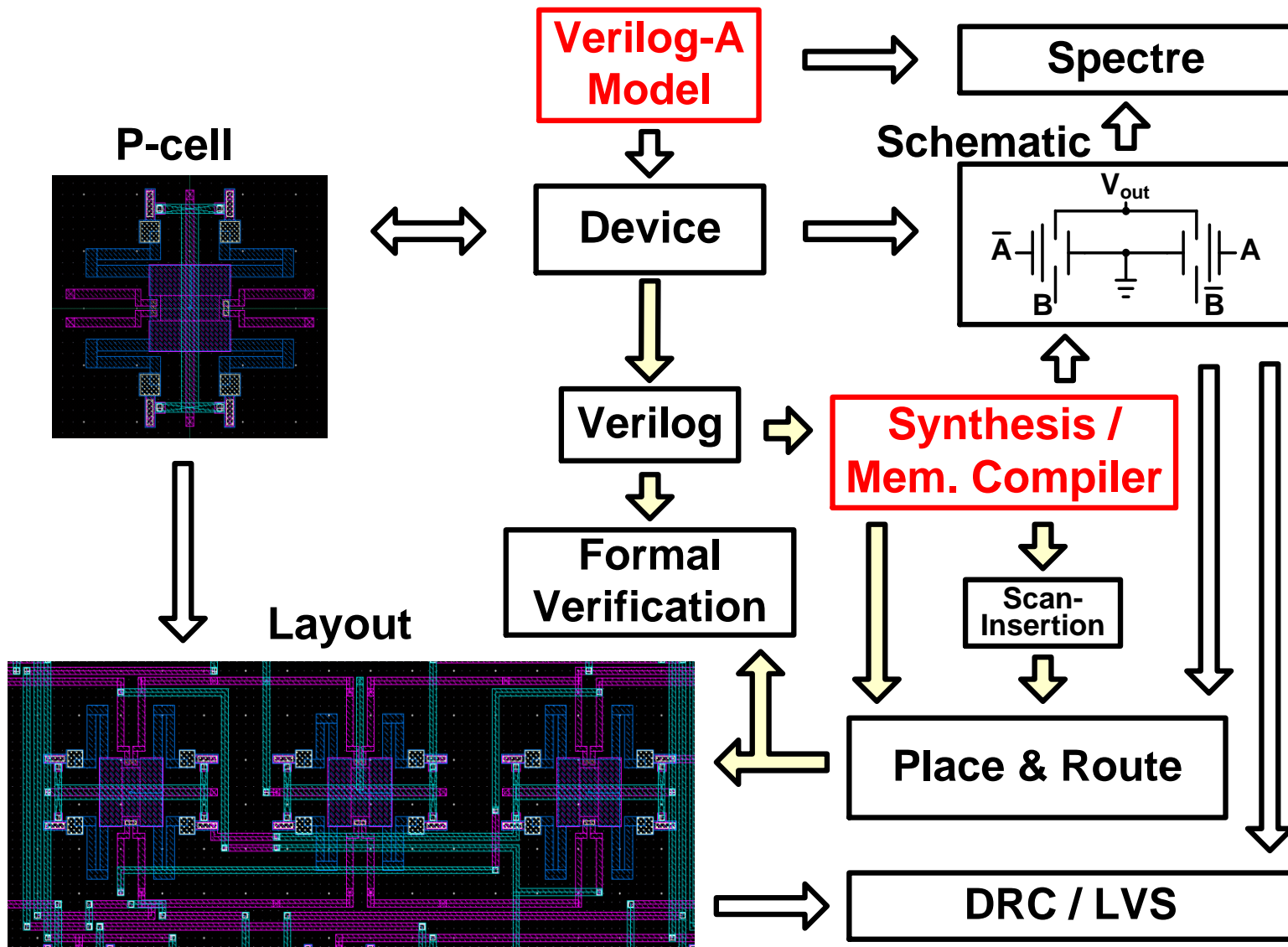


Relay Gate vs. CMOS

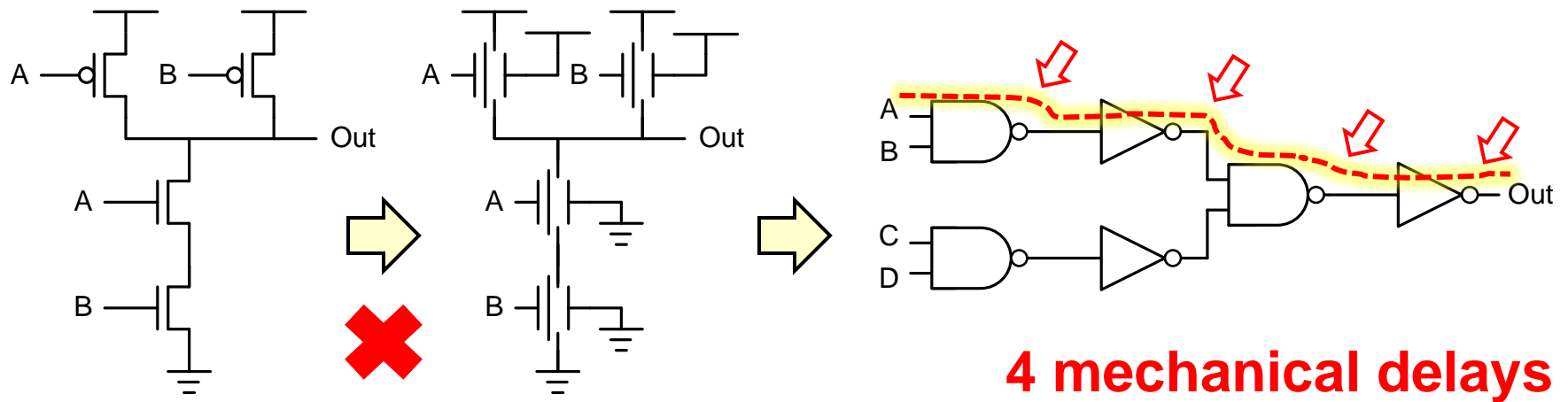- 1 : 1 mapping unacceptable (1 mech. delay per stage)



- Signals propagate through S/D

 


Relay Gate vs. PTL

- Intermediate signals can't drive relay gate



Circuit	Logic Function

 - Inverters cannot be used (add a mech. delay)



(from Yano et al., JSSC 4/90)

Relay-based Synthesis

Goals:










- ❑ Minimize the number of mechanical delays
- ❑ Minimize the number of relay devices

Approach:

- ❑ Work with compound gates
- ❑ Implement node sharing

Types of Relay Devices

Support for three device types

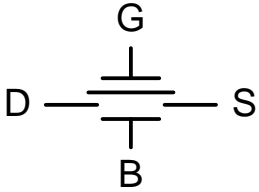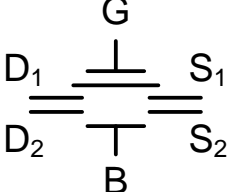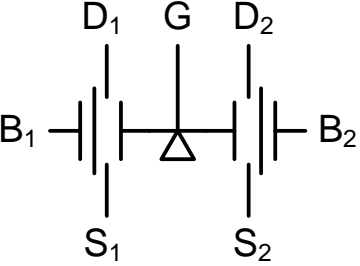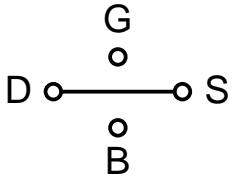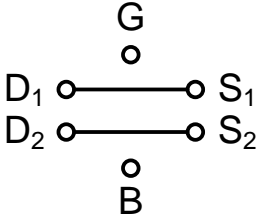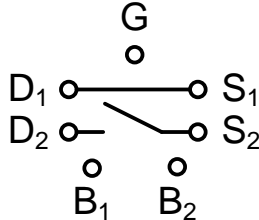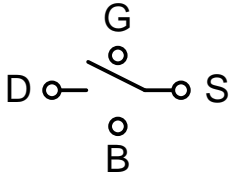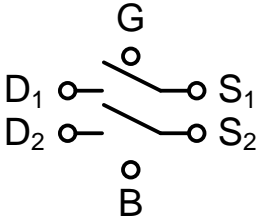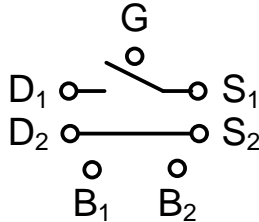
4-Terminal Relay	6-Terminal Relay	Seesaw Relay
		
<p>On State: $G \neq B$</p> 	<p>On State: $G \neq B$</p> 	<p>State 1: $G \neq B_1$</p> 
<p>Off State: $G = B$</p> 	<p>Off State: $G = B$</p> 	<p>State 2: $G \neq B_2$</p> 

Common Device Configurations

	Circuit Symbol	Abbreviated Symbol	Function
4T			0 Activated Pass Gate
			1 Activated Pass Gate
6T			0 Activated Double Pass Gate
			1 Activated Double Pass Gate
Seesaw			Compound Pass Gate


Tree-based Approach

- 1 mechanical delay, large device count

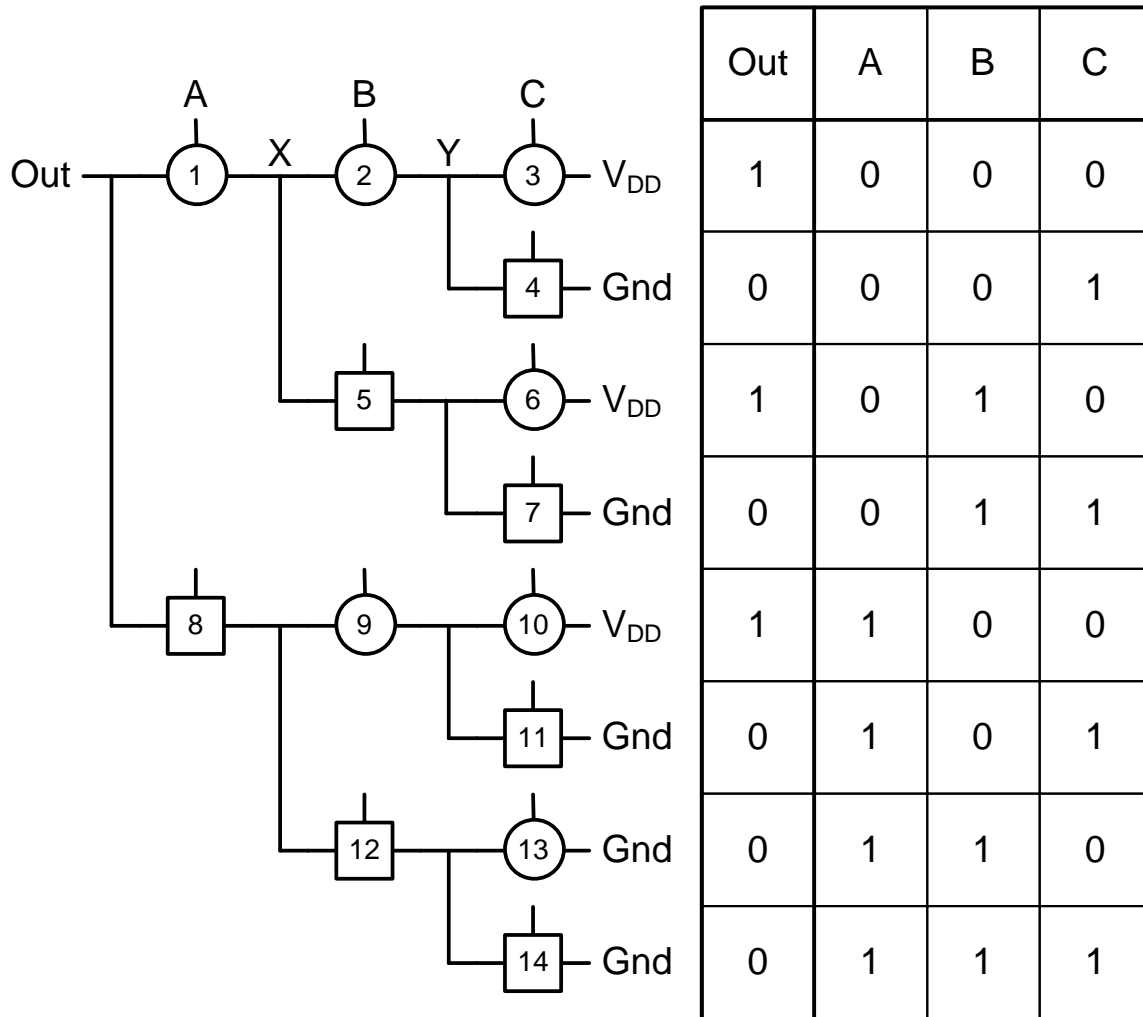

Tree-based Approach

- 1 mechanical delay, large device count

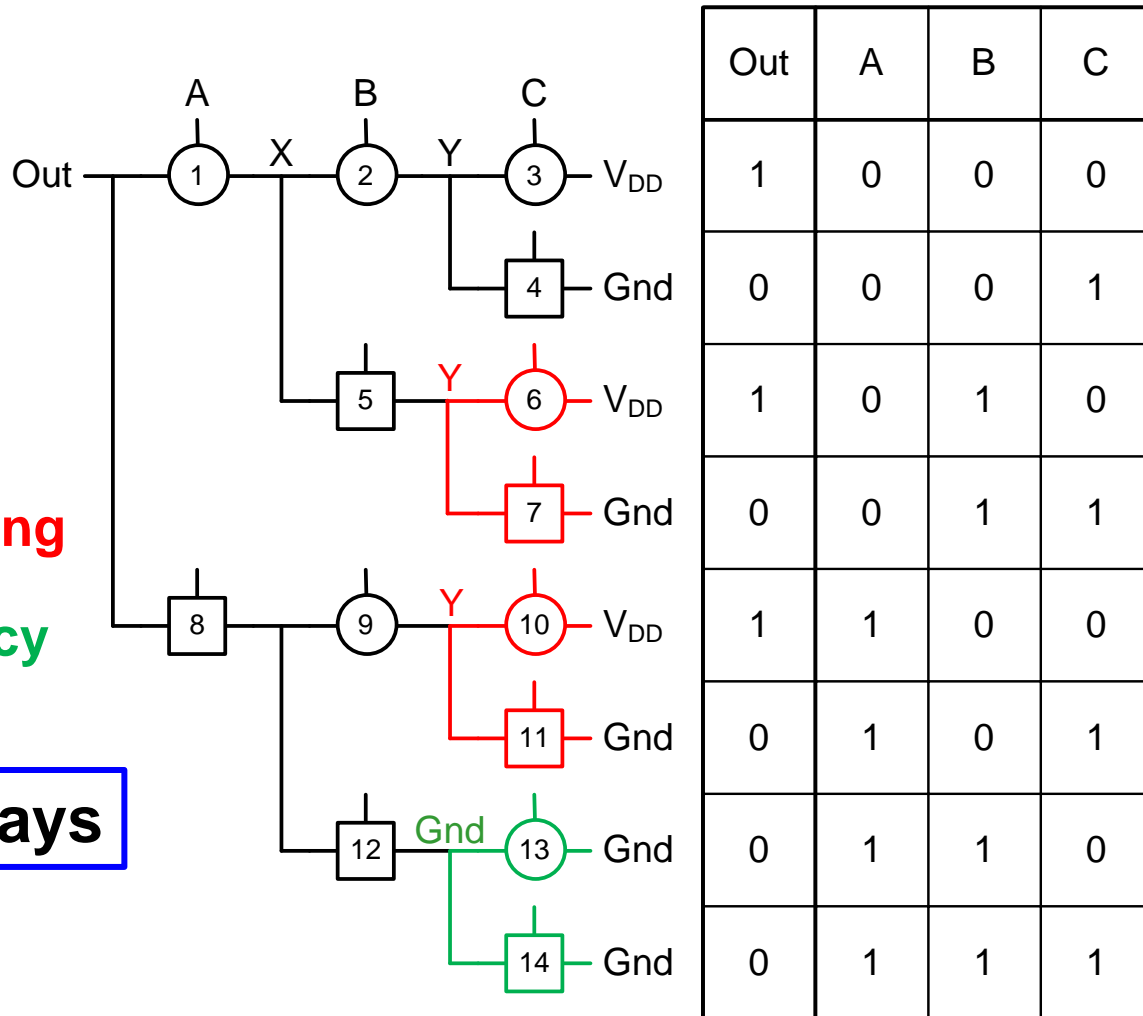

node sharing

redundancy

14 → 8 relays

Truth-Table Reduction

- ❑ Redundancy pruning
 - ❑ Perform K-maps at the truth-table level
 - ❑ 2^N table entries


A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
1	0	0	0
1	1	0	0

A	B	C	Out
0	1	1	1
1	0	1	1
1	1	1	1

Truth-Table Reduction

Redundancy pruning

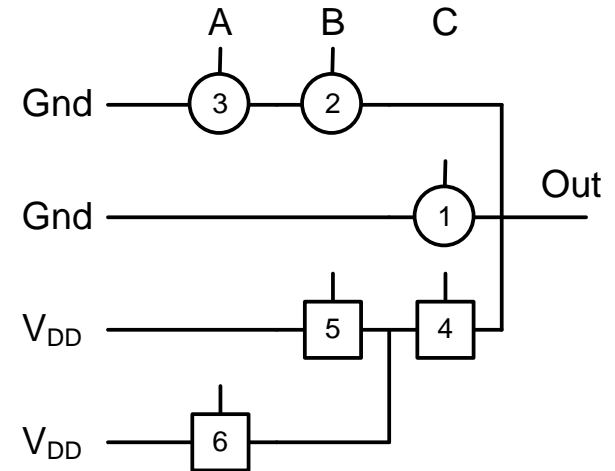- Perform K-maps at the truth-table level
- A “x” value is marked as -1



A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	0
1	0	0	0
1	1	0	0

A	B	C	Out
0	0	-1	0
0	-1	0	0
1	-1	0	0

A	B	C	Out
0	0	-1	0
-1	-1	0	0

A	B	C	Out
0	1	1	1
1	0	1	1
1	1	1	1


A	B	C	Out
-1	1	1	1
1	-1	1	1

A	B	C	Out
-1	1	1	1
1	-1	1	1

2^N table entries


Node Sharing

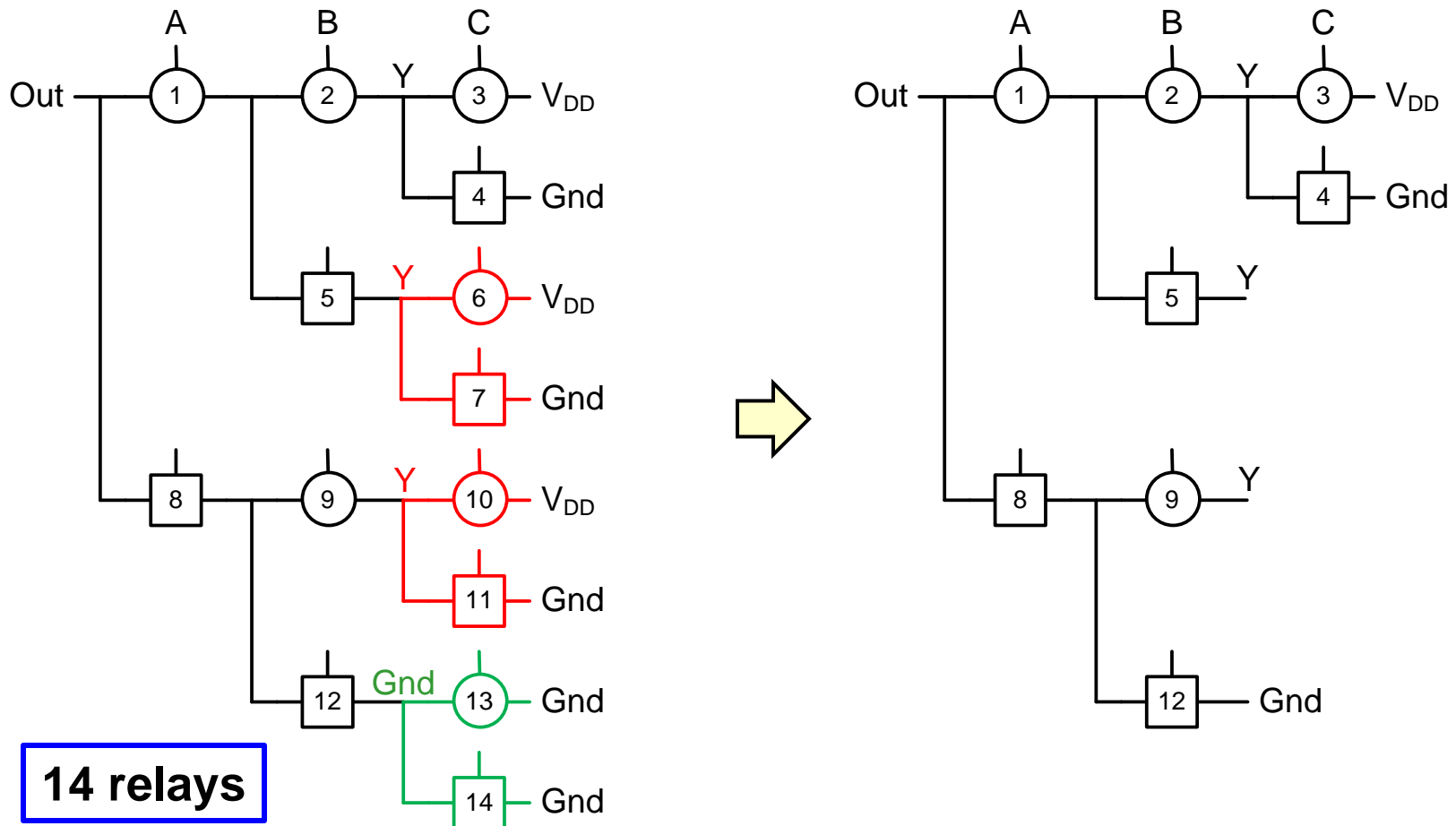- Utilizes common sub-expressions
 - One output shown for simplicity (could be separate trees)




Node Sharing

 - Utilizes common sub-expressions
 - One output shown for simplicity (could be separate trees)




6 relays

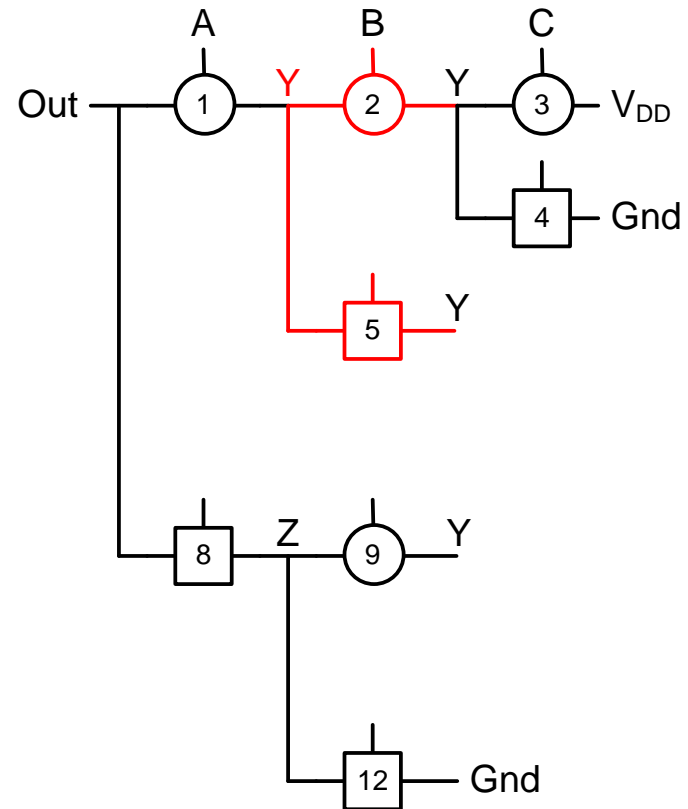

Support for S/D Input

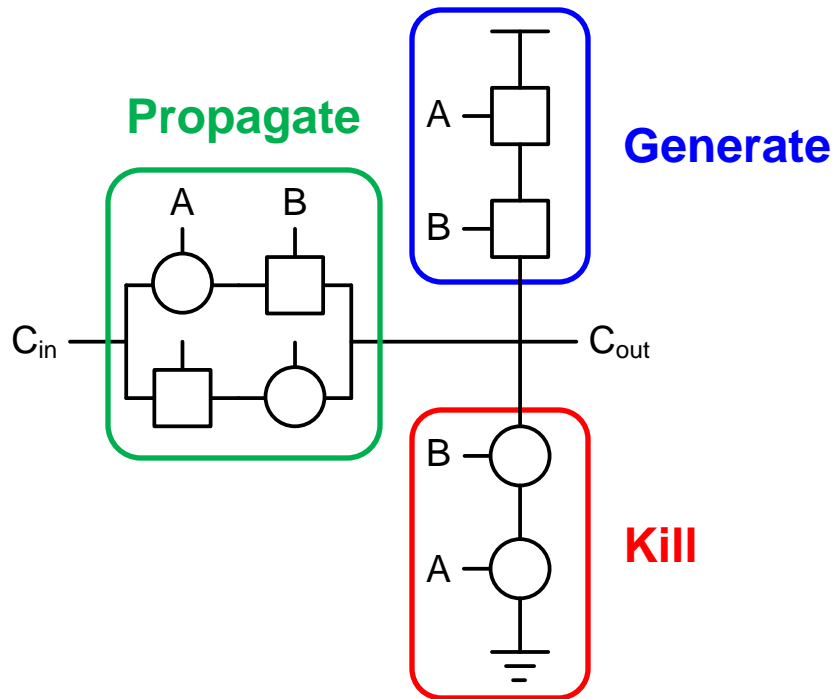- Essential for 0-mechanical-delay concatenation






Adder example

How do we
synthesize for
S/D input?


Support for S/D Input

- Convert to a tree structure

 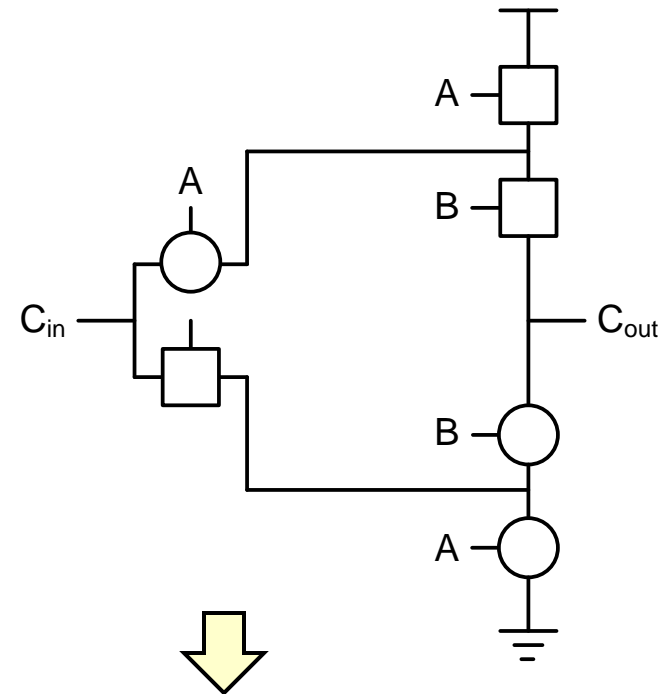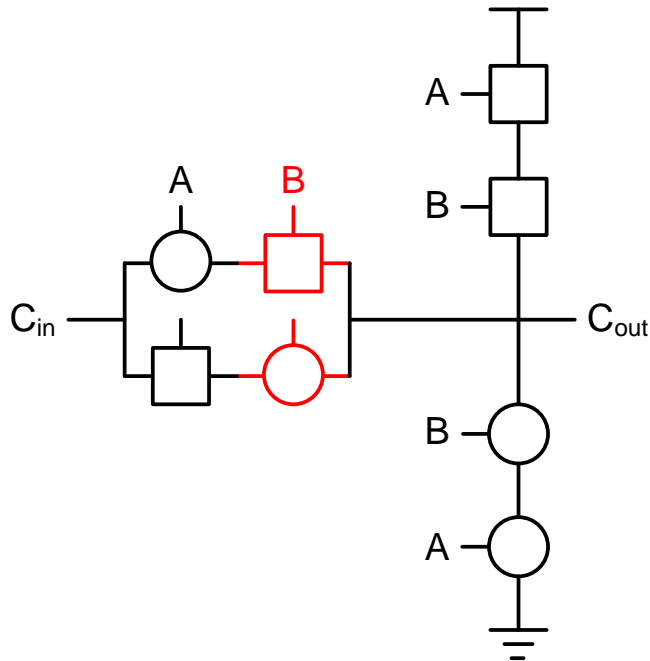

BDD Representation

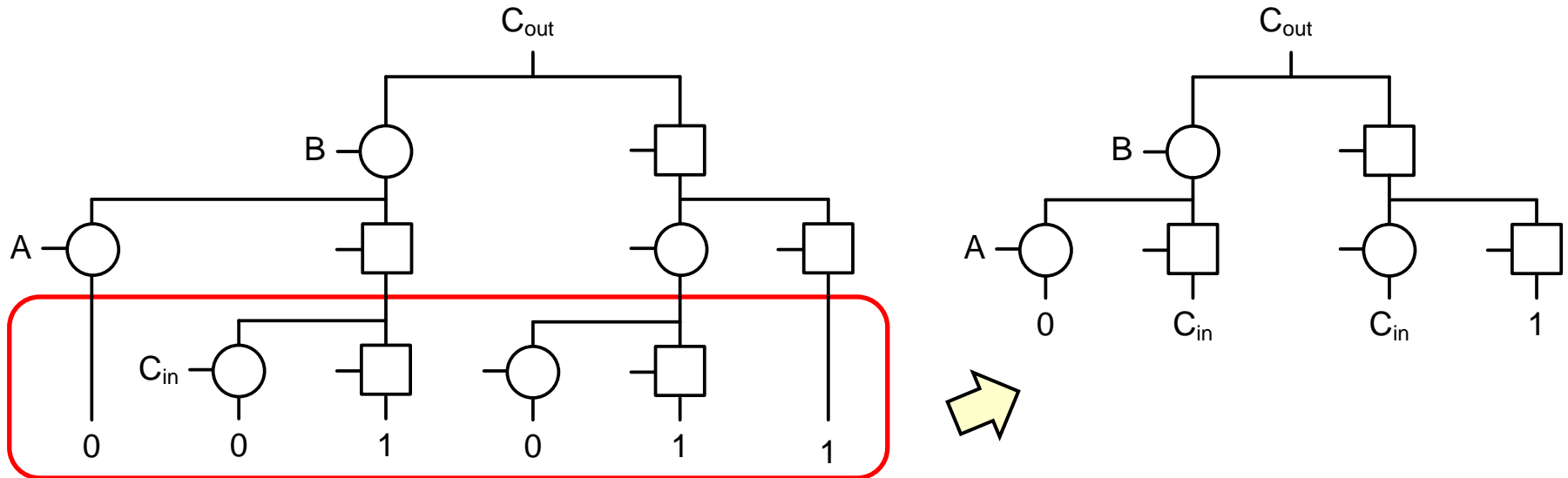- Input on the lowest hierarchy can be merged into S/D




S/D mapping

00	01	10	11
0	C_{in}	$\overline{C_{in}}$	1

Modified-BDD Adder


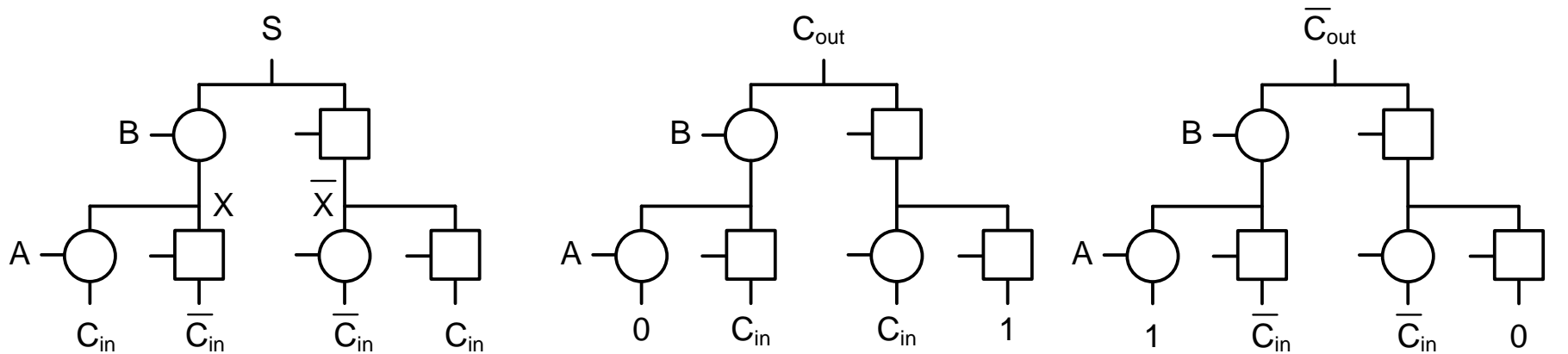
- Generate C_{out} and its complement for ripple carry
 - Cannot insert inverters (gate input = mechanical delay)





Inversion requires tree duplication

Modified-BDD Adder

  - Node sharing can be exploited in some cases



Suitable for node sharing

 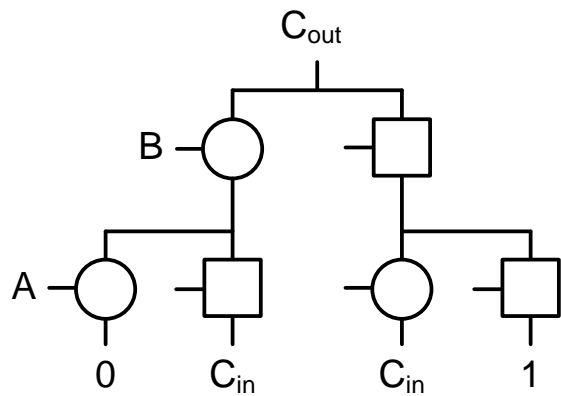

NOT suitable for node sharing

Matlab vs. ABC Tool

□ Runtime comparison (1 mechanical delay)

Design	Matlab	ABC*
1-bit add	0.7 s	0.01 s
4-bit add	20.8 s	0.02 s
8-bit add	2.8 hrs	0.02 s
32-bit add	impractical	0.05 s
64-bit add	impractical	0.16 s
4:1 MUX	0.6 s	0.01 s
8:1 MUX	0.9 s	0.02 s
Instr. decoder	258 s	0.02 s


* w/o sharing algorithm

Matlab tool limited to logic cones with $N \leq 16$ inputs

<http://www.eecs.berkeley.edu/~alanmi/abc>


Synthesis: Remaining Challenges

 - ❑ Node sharing in the BDD
- ❑ Area vs. mechanical delay tradeoff
- ❑ Back-gate input




6T and Seesaw for Low Area

- 2x area reduction compared to 4T

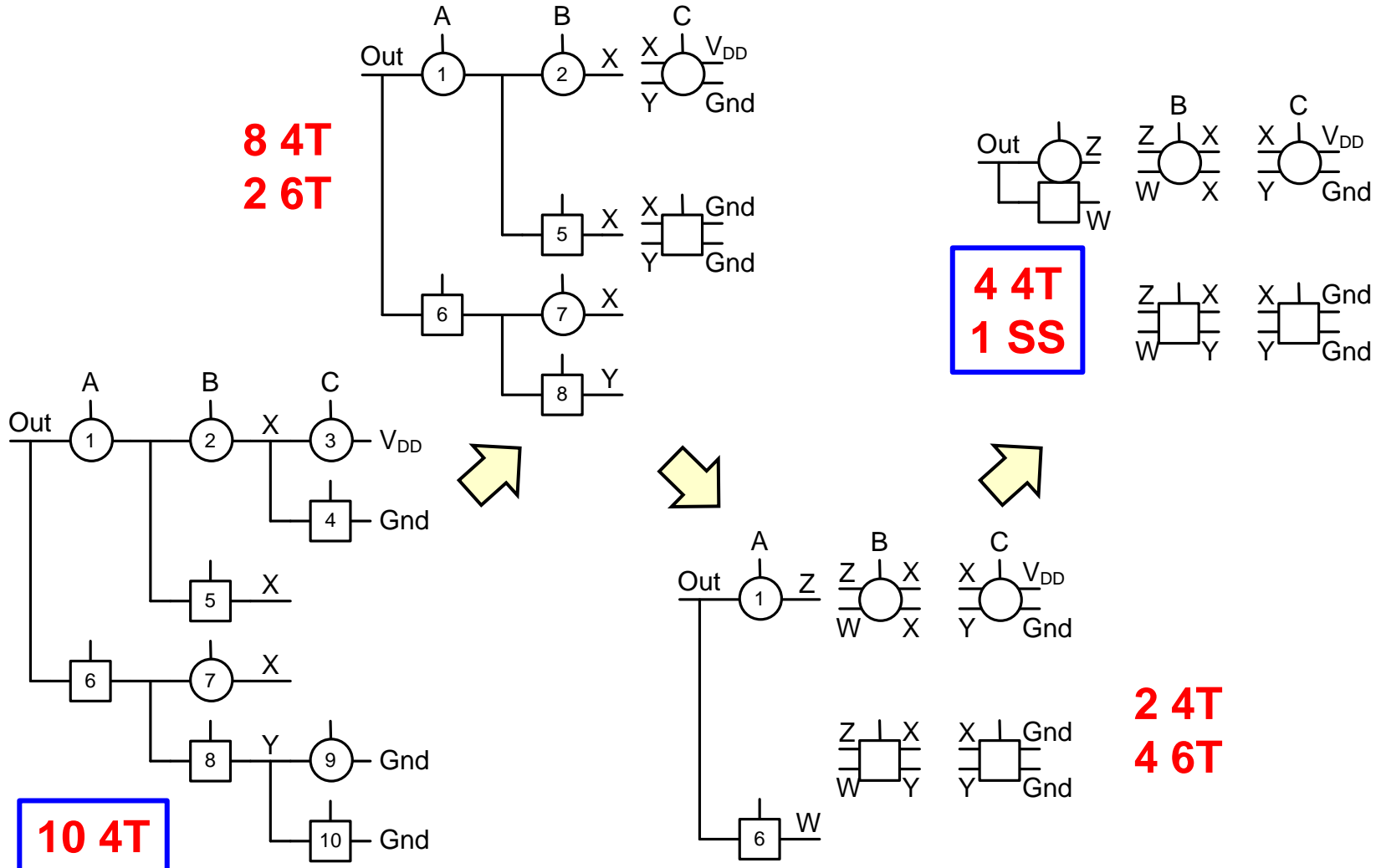


Layout Automation

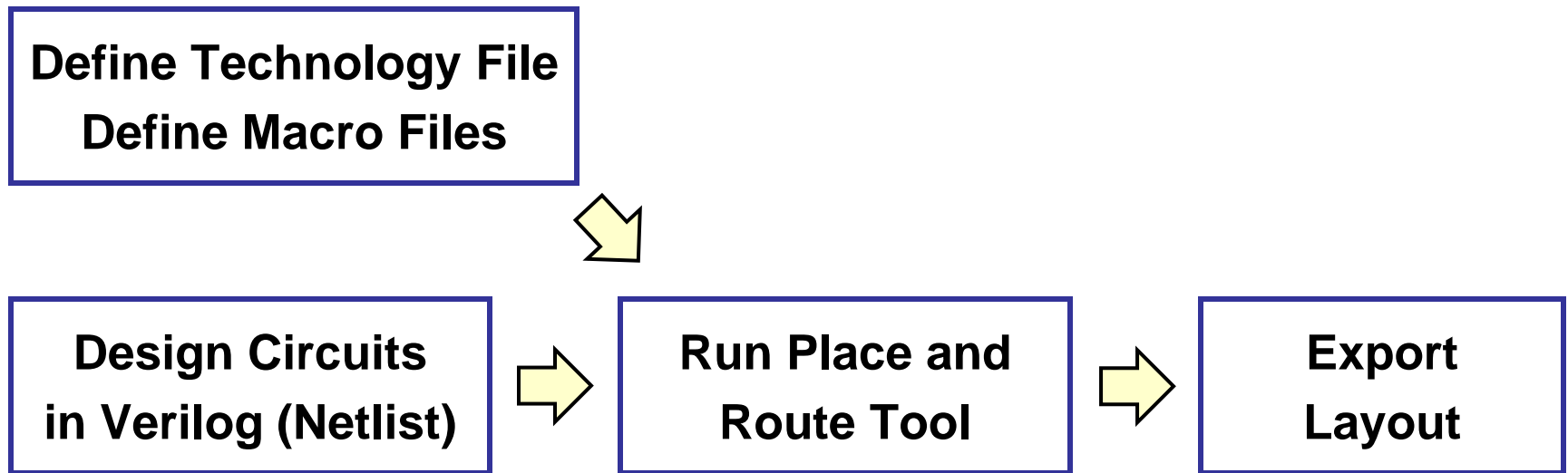- ❑ Using commercial P&R tool (Cadence Encounter)
 - ❑ Define technology file (LEF)
 - ❑ Define “standard-cell” macros (LEF)



Memory Compiler

- Auto-generate memory macros

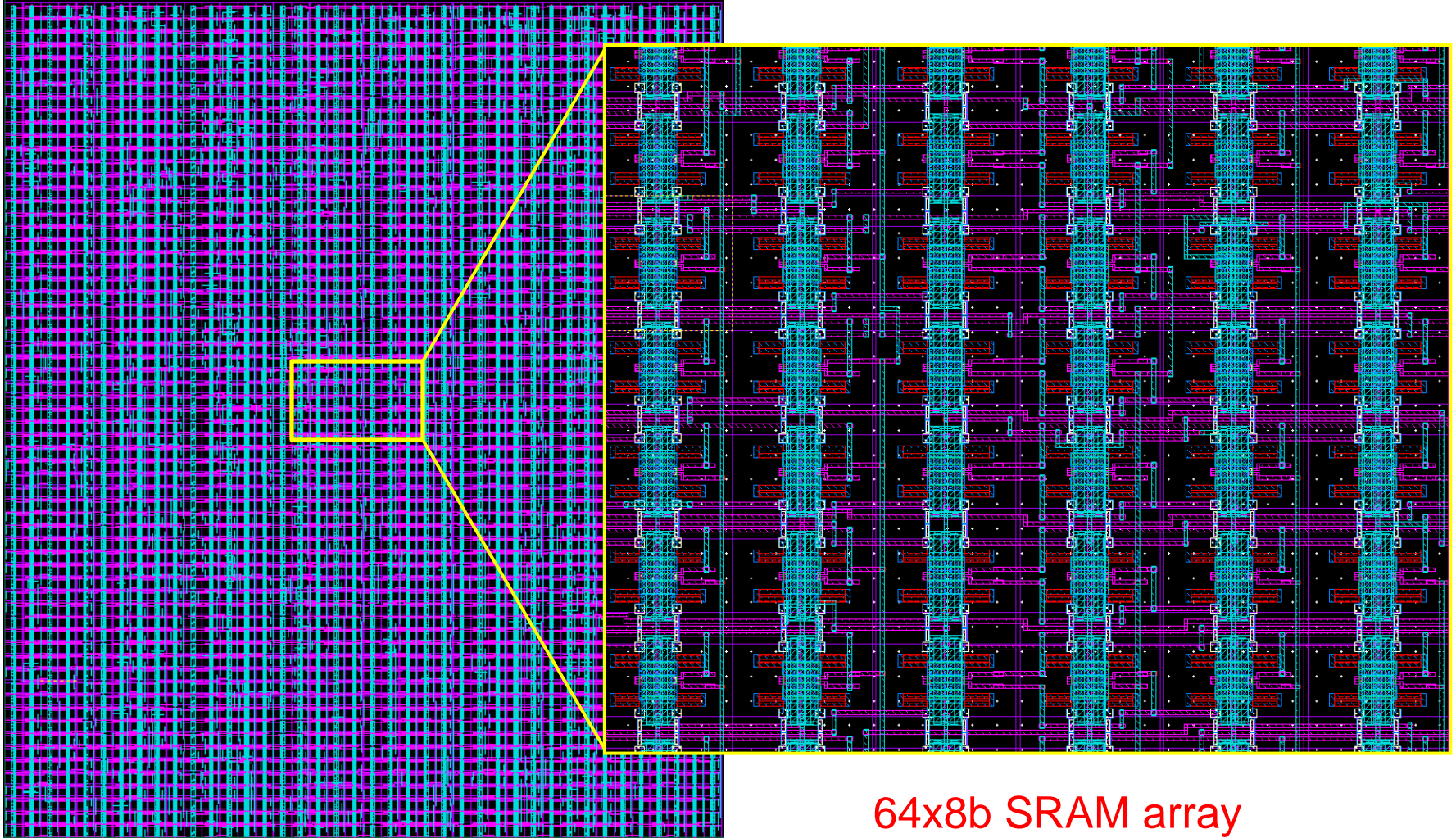

Chip Integration

□ Microcontroller design


- Memory banks (80% area)
- 1 core

□ Design flow

- 85% compiled memories
- 10% logic synthesis (Inst. decode)
- 5% custom design (ALU)

□ Verifications

- DRC, LVS, Formal

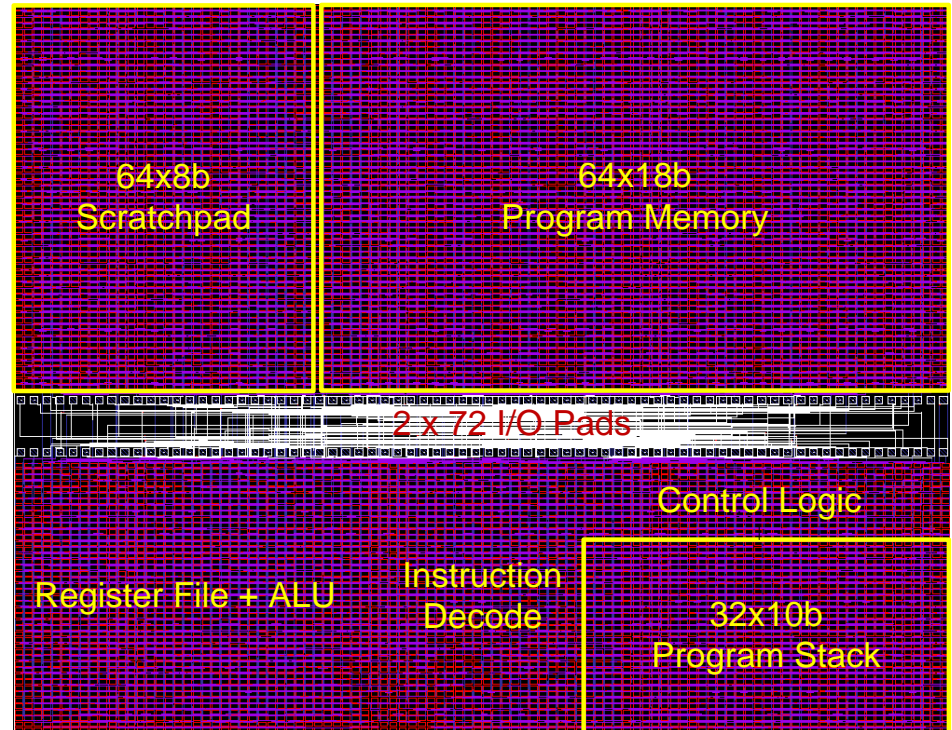

12k relays


DRC Check

- ❑ Automated DRC (compatible with Calibre)
 - ❑ Spacing and geometry rules
 - ❑ Layer-crossing release holes

Example of Metal1 Spacing Rule

```
//*****  
//***** METAL1 Layout Rules *****  
//*****  
  
m1NotGate    = METAL1 NOT GATE  
m1NotDevice  = (METAL1 NOT (SIZE GATE BY 50)) NOT (SIZE BODY BY 47)  
m1Small      = m1NotGate WITH WIDTH < 3  
m1Other      = m1NotDevice WITH WIDTH >= 3  
  
M1Width1    {@ ERROR: Metal1 line width must be 3um or greater.  
             INT m1Small < 3 ABUT>0<90 SINGULAR REGION }  
  
M1Width2    {@ WARNING: Metal1 line width is recommended to be 10um or greater.  
             INT (m1Other NOT (SIZE BODY BY 2)) < 10 ABUT>0<90 SINGULAR REGION }  
  
M1Spacing   {@ ERROR: Metal1 line spacing must be 2um or greater.  
             EXT m1NotGate < 2 ABUT>0<90 SINGULAR REGION }
```

LVS Check

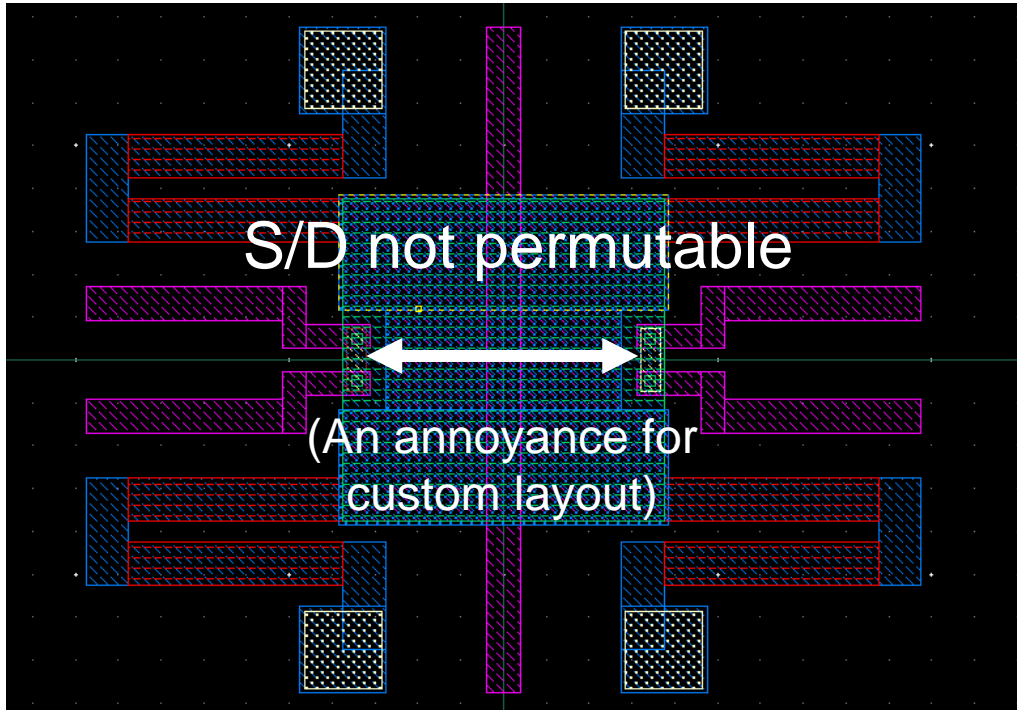

**Use Calibre
for LVS**

- ❑ **Some limitations on what can be recognized/allowed (e.g. S/D permutation)**

Conclusion

- ❑ Relay flow can leverage many features of CMOS design
- ❑ Minimization of mechanical delay and area essential
 - ❑ Biggest challenge for logic synthesis
- ❑ Modified BDD algorithm is a suitable candidate
 - ❑ Create sub-trees to eliminate inverters
 - ❑ Absorb critical-path input as S/D
 - ❑ Absorb common sub-trees through node sharing

Relay VLSI is here!